CSC258: Computer Organization

Devices

Your Mission ...

• Generate the circuit that adds two one-bit numbers.

- Start with a truth table.
- Optimize the formula.
- Draw the circuit.

Where are we?

- Our goal, eventually, is to build a simple processor.
- For that, we need:
 - The ability to execute simple operations (like "add")
 - The ability to choose between values.
 - Storage for a small number of values (variables)
 - A circuit to process instructions from the user.



How do we get there?

We can already do NAND -- and that's everything right?

 We'll look at shifters and adders in a couple of weeks, and we'll use those to create an ALU.

Where are we?

- Our goal, eventually, is to build a simple processor.
- For that, we need:
 - The ability to execute simple operations (like "add")
 - The ability to choose between values.
 - Storage for a small number of values (variables)
 - A circuit to process instructions from the user.



Multiplexer (Mux)

- Sometimes, we need "select" or "choose"
- A mux takes multiple inputs and a selector input

The selector chooses which input to



... and the Reverse

- Since we "mux", we should be able to "demux"
 - Take one input and a selector, and produce the input on one of the outputs

- The text also covered encoders and decoders.
 - An encoder takes 2^N inputs and produces a N-bit (compacted) output
 - A decoder takes an N-bit input and produces 2^N (extracted) outputs

Where are we?

- Our goal, eventually, is to build a simple processor.
- For that, we need:
 - The ability to execute simple operations (like "add")
 - The ability to choose between values.
 - Storage for a small number of values (variables)
 - A circuit to process instructions from the user.

How do we get there?

We need some device that can store data.

 We also need some concept of "time", so we know when to store new data.

• We'll start putting together these pieces today.



Storing Data

 Our circuits so far provide an output given some inputs



- The other half of the equation is storage
 - Use feedback to "freeze" a value
- These are SR latches
 - They rely on feedback.



Your Mission ...

Provide the truth table and the circuit for an SR latch.

SR Latches

- R is labeled "reset"
- S is labeled "set"



- When R is high, Q becomes 0
- When S is high, Q becomes I
- Otherwise, Q keeps its previous value.
- RSQ \neg Q00Q \neg Q0110100111??

Your Mission ...

Add a clock input to your latch truth table.

Think about what you want the clock input to mean: when does the device trigger?

Adding Timing to Circuits



- Idea: We need to hold a value long enough for it to stabilize and to use it for computation
- Solution: Add a "clock" that tells all of the latches in the circuit to change their value
 - Pulse width must be large enough to let values stabilize
 - Period must be long enough to let computation finish

Gated Latches





CI	S	R	Q	٦Q
0	X	X	Q	¬Q
1	0	0	Q	¬Q
Т	0	1	0	Т
Т	1	0	1	0
1	1		?	?

Characteristic Equation

- Every gated-latch can be defined as a function based on time
 - This is called its characteristic equation.

• For the SR gated latch: $Q(t + I) = S(t) + \neg R(t)Q(t)$

 S
 R
 Q(t+1)

 0
 0
 Q(t)

 0
 I
 0

 I
 0
 I

 I
 I
 ?

II Transition Problems

- For an SR latch, the "II" state is unstable
 - Both Q and Q' are 0
 - A transition to the "00" state yields undefined outputs

Solution: Eliminate the "II" state

D Latch

- Instead of two inputs, the D latch has one
 - D stands for "data"

- Easily made from an SR latch
 - How?

 D
 Q
 Q'

 0
 0
 1

 1
 1
 0

Transparency

- All latches are "transparent"
- When the input changes, the output immediately changes (within some propagation delay)

- Problem: What happens if an input changes in the middle of a clock cycle?
 - This happens often! Many circuits use latches that feed into other latches
 - If the cycle is longer than the propagation delay, problems occur

Master-Slave Flip-Flop

- Output of the flipflop is delayed to break a circuit into a sequence of circuits operating in parallel.
- Prevents value from being propagated early





Latches and Waveforms



