 


*2 marks***Part (d) Timing**

Given the input waveform below, sketch the output, Q , of an SR latch and SR flip-flop.

*2 marks***Part (e) FSMs and Processors**

Explain how the MIPS processor in the textbook is a finite state machine.